



Tanta University



Faculty of Engineering

Electrical Power and Machines Department
1st Year (Electrical) 2012/2013 (2nd Term)
Electrical Circuits (2) (EPM1203)

Sheet (3)

Balanced Three-Phase Circuits

1) For each set of voltages, **state** whether or not the voltages form a *balanced three-phase set*. If the set is balanced, **state** whether the phase sequence is *positive* or *negative*.
If the set is not balanced, **explain why?**

- a) $v_a = 139 \cos 377 t \text{ V}$, $v_b = 139 \cos(377 t + 120^\circ) \text{ V}$, $v_c = 139 \cos(377 t - 120^\circ) \text{ V}$.
- b) $v_a = 381 \cos 377 t \text{ V}$, $v_b = 381 \cos(377 t + 240^\circ) \text{ V}$, $v_c = 381 \cos(377 t + 120^\circ) \text{ V}$.
- c) $v_a = 2771 \sin(377 t - 30^\circ) \text{ V}$, $v_b = 2771 \cos 377 t \text{ V}$, $v_c = 2771 \sin(377 t + 210^\circ) \text{ V}$.
- d) $v_a = 170 \sin(\omega t + 30^\circ) \text{ V}$, $v_b = -170 \cos(\omega t) \text{ V}$, $v_c = 170 \cos(\omega t + 60^\circ) \text{ V}$.

2) A balanced three-phase circuit has the following characteristics:

- Y-Y connected;
- The line voltage at the source V_{ab} is $240 \sqrt{3} \angle 90^\circ \text{ V}$;
- The phase sequence is negative;
- The line impedance is $4 + j5 \Omega/\Phi$. The load impedance is $76 + j55 \Omega/\Phi$

i) **Draw** the single phase equivalent circuit for the a-phase.

ii) **Calculate:**

- a) The line currents.
- b) The line voltages at the load terminals.
- c) The phase voltages at the load terminals.
- d) The line voltages at the load terminals.
- e) The phase voltages at the source terminals.
- f) The line voltages at the source terminals.
- g) Repeat a-f for positive phase sequence.

3) The magnitude of the line voltage at the terminals of a balanced Y-connected load is 6600 V. The load impedance is $240 - j70 \Omega/\Phi$. The load is fed from a line that has an impedance of $0.5 + j4 \Omega/\Phi$.

- a) **What** is the magnitude of the line current?
- b) **What** is the magnitude of the line voltage at the source terminals?

4) A balanced, three-phase circuit is characterized as follows:

- Y- Δ connected;
- Source voltage in the c-phase is $20 \angle -90^\circ$ V;
- Source phase sequence is ABC;
- Line impedance is $1 + j3 \Omega/\Phi$;
- Load impedance is $117 - j99 \Omega/\Phi$.

i) **Draw** the single phase equivalent circuit for the a-phase.

ii) **Calculate**:

- a) The line currents.
- b) The line voltages at the load terminals.
- c) The phase voltages at the load terminals.
- d) The line voltage at the load terminals.
- e) The phase voltages at the source terminals.
- f) The line voltages at the source terminals.
- c) The a-phase line voltage for the three phase load.
- g) Repeat a-f for ACB sequence.

5) An acb sequence balanced three-phase Y-connected source supplies power to a balanced, three-phase Δ -connected load with an impedance of $12 + j9 \Omega/\Phi$. The source voltage in the b-phase is $240 \angle 50^\circ$ V. The line impedance is $1 + j1 \Omega/\Phi$.

Draw the single phase equivalent circuit for the a-phase *and use it to find* the current in the a-phase of the load.

6) A balanced Δ -connected load has an impedance of $864 - j252 \Omega/\Phi$. The load is fed through a line having an impedance of $0.54 - j4 \Omega/\Phi$. The phase voltage at the terminals of the load is 69 kV. The phase sequence is positive. Use v_{ab} as the reference.

- a) **Calculate** the three phase currents of the load.
- b) **Calculate** the three line currents.
- c) **Calculate** the three line voltages at the sending end of the line.

7) In a balanced three-phase system, the source is a balanced Y with an ABC phase sequence and a line voltage $V_{ab} = 208 \angle 50^\circ$ V. The load is a balanced Y in parallel with a balanced Δ . The phase impedance of the Y is $4 + j3 \Omega/\Phi$. the phase impedance of the Δ is $3 - j9 \Omega/\Phi$. and the line impedance is $1.4 + j0.8 \Omega/\Phi$.

Draw the single phase equivalent circuit *and use it to calculate* the line voltage at the load in the a-phase.

8) A balanced three-phase Δ -connected source is shown in Fig.1

a) **Find** the Y-connected equivalent circuit.

b) **Show** that the Y-connected equivalent circuit delivers *the same open-circuit voltage* as the original Δ -connected source.

c) Apply an *external short circuit* to the terminals A, B, and C. Use the Δ -connected source to **find** the three line currents I_{Aa} , I_{Bb} , and I_{Cc} .

d) **Repeat** (c) but use the Y-equivalent source to **find** the three line currents.

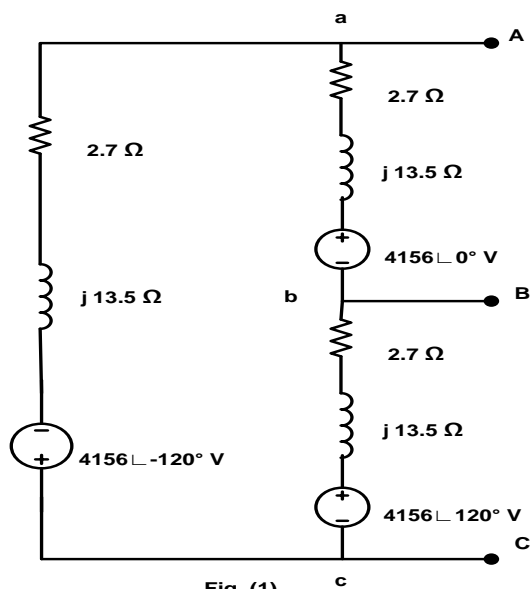


Fig. (1)

9) In a balanced three-phase system, the source has an ABC sequence, is Y- connected, and $V_{an} = 120 \angle 20^\circ$ V. The source feeds **two loads**, both of which are Y-connected. The impedance of load 1 is $8 + j6 \Omega/\Phi$. The complex power for the a-phase of load 2 is $600 \angle 36^\circ$ VA.

Find the total complex power supplied by the source.

10) A balanced three-phase distribution line has an impedance of $1 + j8 \Omega/\Phi$. This line is used to supply three balanced three-phase loads that are connected in parallel.

The **three loads** are:

load 1 = 120 kVA at 0.96 pf lead,

load 2 = 180 kVA at 0.80 pf lag, and

load 3 = 100.8 kW and 15.6 kVAR (magnetizing).

The magnitude of the line voltage at the terminals of the loads is $2400 \sqrt{3}$ V.

a) **What** is the magnitude of the line voltage at the sending end of the line?

b) **What** is the percent efficiency of the distribution line with respect to average power?

11) Three balanced three-phase loads are connected in parallel. load 1 is Y-connected with an impedance of $400 + j300 \Omega/\Phi$; load 2 is Δ -connected with an impedance of $2400 - j1800 \Omega/\Phi$; and load 3 is $72.8 + j2203.2 \text{ kVA}$. The loads are fed from a distribution line with an impedance of $2 + j16 \Omega/\Phi$. The magnitude of the line-to-neutral voltage at the load end of the line is $24\sqrt{3} \text{ kV}$.

- a) **Calculate** the total complex power at the sending end of the line.
- b) **What** percentage of the average power at the sending end of the line is delivered to the loads?

12) The complex power associated with each phase of a balanced load is $144 + j192 \text{ kVA}$. The line voltage at the terminals of the load is 2450 V .

- a) **What** is the magnitude of the line current feeding the load?
- b) The load is delta connected, and the impedance of each phase consists of a resistance in parallel with a reactance. **Calculate** R and X.
- c) The load is wye connected, and the impedance of each phase consists of a resistance in series with a reactance. **Calculate** R and X.

13) A balanced bank of delta-connected capacitors is connected in parallel with the load described in Problem 12. The effect is to place a capacitor in parallel with the load in each phase. The line voltage at the terminals of the load thus remains at 2450 V . The circuit is operating at a frequency of 60 Hz . The capacitors are adjusted so that the magnitude of the line current feeding the parallel combination of the load and capacitor bank is at its minimum.

- a) **What** is the size of each capacitor in microfarads?
- b) **Repeat (a)** for **wye-connected** capacitors.
- c) **What** is the magnitude of the line current?